

## Experiment No. : 8

**Aim:** To Study of flip flop IC.

### Theory:

A flip flop is an electronic circuit with two stable states that can be used to store binary data. The stored data can be changed by applying varying inputs. Flip-flops and latches are fundamental building blocks of digital electronics systems used in computers, communications, and many other types of systems.

1. R-S flip flop
2. D flip flop
3. J-K flip flop
4. T flip flop

#### 1) RS flip flop

The basic NAND gate RS flip flop circuit is used to store the data and thus provides feedback from both of its outputs again back to its inputs. The RS flip flop actually has three inputs, SET, RESET and clock pulse.

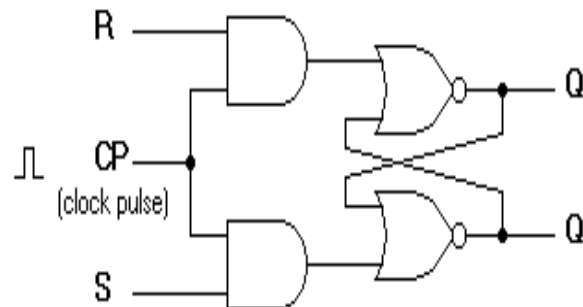


Figure-1:R-S flip flop circuit diagram



Input			Output	
D	reset	clock	Q	Q'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

Figure-4:Characteristics table of D flip flop

### 3) J-K flip flop

In a RS flip-flop the input  $R=S=1$  leads to an indeterminate output. The RS flip-flop circuit may be re-joined if both inputs are 1 than also the outputs are complement of each other as shown in characteristics table below.

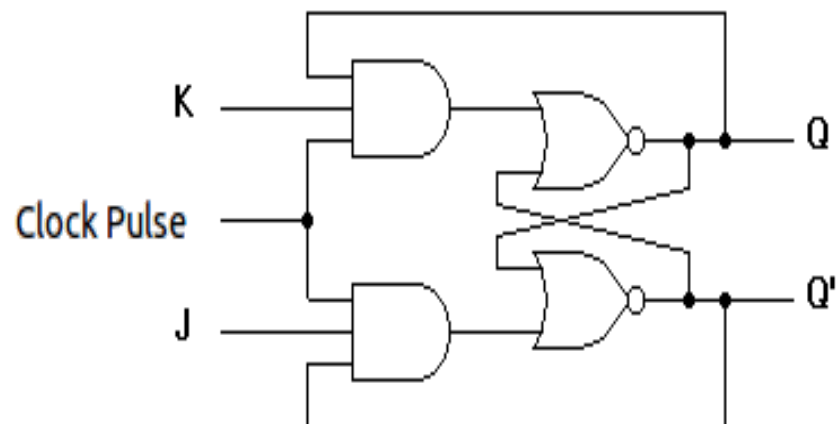


Figure-5:Circuit diagram of J-K flip flop








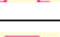

Trigger	Inputs		Output				Inference
			Present State		Next State		
CLK	J	K	Q	Q'	Q	Q'	
	x	x	-		-		Latched
	0	0	0	1	0	1	No Change
			1	0	1	0	
	0	1	0	1	0	1	Reset
			1	0	0	1	
	1	0	0	1	1	0	Set
			1	0	1	0	
	1	1	0	1	1	0	Toggles
			1	0	0	1	

Figure-6:Characteristics table of J-K flip flop

#### 4) T flip flop

T flip-flop is known as toggle flip-flop. The T flip-flop is modification of the J-K flip-flop. Both the JK inputs of the JK flip – flop are held at logic 1 and the clock signal continuous to change as shown in table below.

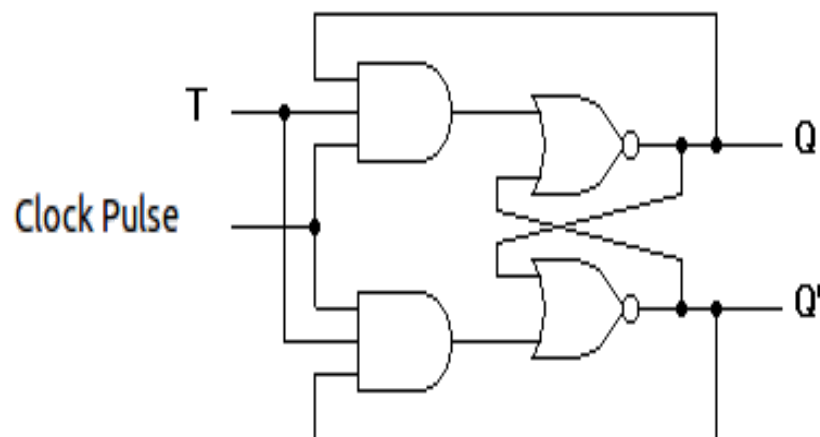


Figure-7:Circuit diagram of T flip flop

**T flip-flop**

<b>T</b>	<b>Clock</b>	<b>Q</b>	<b>Q'</b>
<b>0</b>	↑	Q	Q'
<b>1</b>	↑	Q'	Q
<b>x</b>	↓	Q	Q'

Figure-8:Characteristics table of T flip flop

Conclusion:

Thus Studied of flip flop IC.